

MULTIMEDIA



UNIVERSITY

STUDENT ID NO

--	--	--	--	--	--	--	--	--	--

# MULTIMEDIA UNIVERSITY

## SUPPLEMENTARY EXAMINATION

TRIMESTER 1, 2015 / 2016

### PPH0135 - ELECTRICITY AND MAGNETISM (Foundation in Engineering)

18 NOV 2015  
9.00 AM – 11.00 AM  
(2 HOURS)


---

#### INSTRUCTIONS TO STUDENT


1. This question paper consists of **FIVE (5)** printed pages excluding the cover page and appendices, with **FOUR (4)** questions.
  2. Answer **ALL** questions. The distribution of the marks for each question is given.
  3. Please write all your answers in the answer booklet provided.
-

**QUESTION 1 (15 marks)**

- a) **Figure Q1.1** shows a strip of silver with dimensions of  $50.0\text{ mm} \times 20.0\text{ mm} \times 500.0\mu\text{m}$ , is placed in a magnetic field ( $B = 0.5\text{ T}$ ) directed perpendicular to the plane of the silver strip. A current  $I = 12\text{ A}$  is sent down the strip as shown in the figure. If the electron density of silver is  $5.86 \times 10^{28}$  per  $\text{m}^3$ , determine
- the drift velocity of electrons. (2 marks)
  - the magnitude and direction of the electric field in the strip. (2 marks)
  - the reading of the voltmeter  $V$ . (1 mark)
  - which side of the voltmeter is at the lower potential. (1 mark)

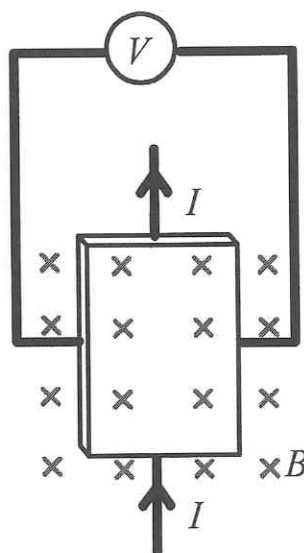
**Figure Q1.1****Continued...**

- b) **Figure Q1.2** shows an electron moves in a circle of radius  $R$  in a uniform magnetic field  $B$ , directed out of the page.

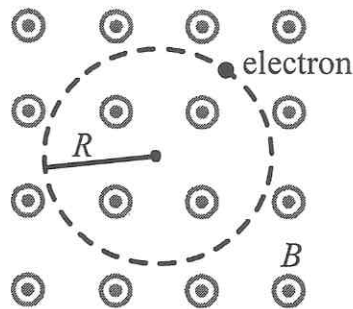

**Figure Q1.2**

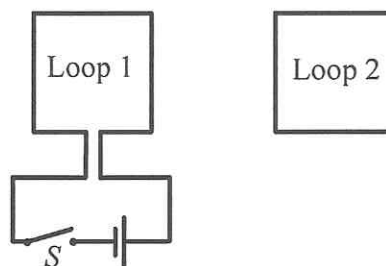- Does the electron move clockwise or counter clockwise?  
(1 mark)
  - Derive an expression for the time taken for the electron to make one complete revolution.  
(3 marks)
  - If  $B = 0.2 \text{ T}$ , determine the value in part (ii).  
(1 mark)
- c) **Figure Q1.3** shows two conducting loops placed in the same plane. If switch  $S$  is closed,
- what is the direction of current flowing in loop 2? Explain.  
(3 marks)
  - does the the current in loop 2 flow for only a short moment , or does it continue?  
(1 mark)

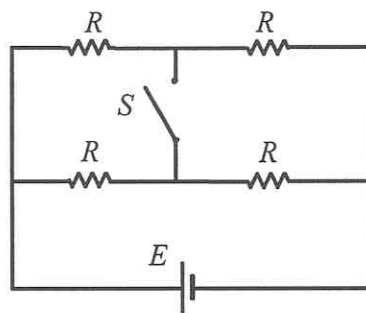


**Figure Q1.3**


Continued...

**QUESTION 2 (15 marks)**

- a) A battery is connected to a resistive load that has a resistance of  $20.0\ \Omega$ . A voltmeter across the battery reads  $7.8\ \text{V}$  when the load is in place and  $9.0\ \text{V}$  when the load is removed. Determine the internal resistance of the battery. (3 marks)
- b) Two tungsten wires, one with a diameter double of the other, have the same current flowing through them. If the drift speed of the thicker wire is  $v_1$ , and the drift speed of the thinner wire is  $v_2$ , calculate the ratio of the drift speeds. (3 marks)
- c) Four identical resistors are connected to a battery as shown in **Figure Q2.1**. When switch  $S$  is open, the current through the battery is  $I_0$ . Calculate the current flows through the battery when the switch is closed. Give your answer in terms of  $I_0$ . (3 marks)


**Figure Q2.1**

- d) Use Thevenin's theorem to find current through and voltage across  $R_1$  in **Figure Q2.2**. Provide Thevenin equivalent circuit in your answer. (6 marks)

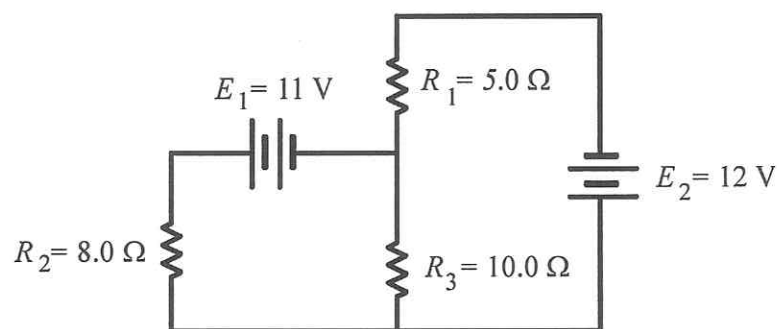**Figure Q2.2****Continued...**

**QUESTION 3 (10 marks)**

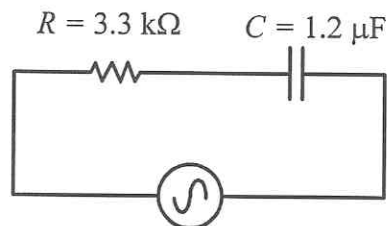**Figure Q3** shows a series RC circuit. The rms voltages across the resistor and the capacitor are the same.

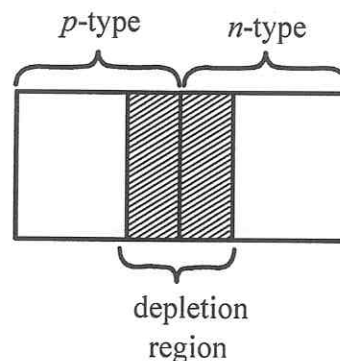


**Figure Q3**

- a) What is the frequency of the source? (2 marks)
- b) Write the rms voltages across the resistor and the capacitor in terms of the rms voltage of the source. (2 marks)
- c) What is the impedance of the circuit? (2 marks)
- d) What is the phase angle between the source voltage and current? Which leads? (2 marks)
- e) Draw a phasor diagram for the circuit. (2 marks)

**QUESTION 4 (10 marks)**

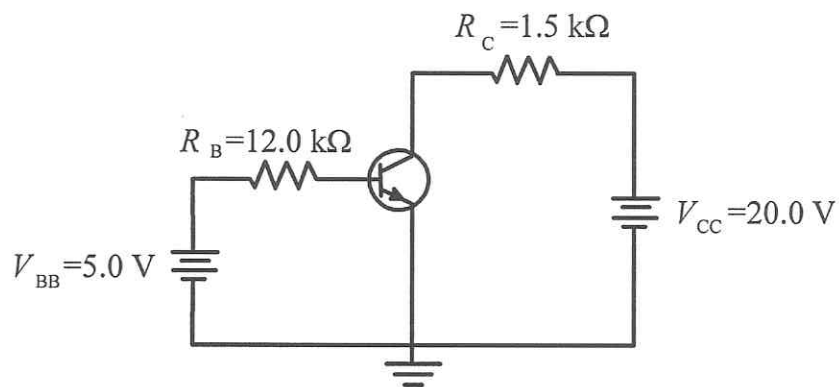
- a) **Figure Q4.1** shows a diagram of unbiased *pn* junction in equilibrium. The shaded area represents depletion region.



**Figure Q4.1**

**Continued...**

- i. What is the net charge of the  $pn$  junction? (1 mark)
  - ii. What is the net charge of the  $p$ -type? (1 mark)
  - iii. What is the net charge of the  $n$ -type? (1 mark)
  - iv. Does a  $pn$  junction have a capacitance behavior associated to it? Explain. (2 marks)
- a) Find the magnitude of  $I_B$ ,  $I_E$  and  $I_C$  in **Figure Q4.2**, given that  $\alpha_{dc} = 0.98$ . Assume that the transistor is of germanium (Ge) type. (5 marks)

**Figure Q4.2****Continued...**

## APPENDIX 1

### Physical Constants

Quantity	Symbol	Value
Electron mass	$m_e$	$9.11 \times 10^{-31} \text{ kg}$
Proton mass,	$m_p$	$1.67 \times 10^{-27} \text{ kg}$
Elementary charge	$e$	$1.602 \times 10^{-19} \text{ C}$
Gravitational constant	$G$	$6.67 \times 10^{-11} \text{ N.m}^2/\text{kg}^2$
Gas constant	$R$	$8.314 \text{ J/K.mol}$
Hydrogen ground state	$E_0$	$-13.6 \text{ eV}$
Boltzmann's constant	$k_B$	$1.38 \times 10^{-23} \text{ J/K}$
Compton wavelength	$\lambda_c$	$2.426 \times 10^{-12} \text{ m}$
Planck's constant	$h$	$6.626 \times 10^{-34} \text{ J.s}$
Speed of light in vacuum	$c$	$3.0 \times 10^8 \text{ m/s}$
Rydberg constant	$R_H$	$1.097 \times 10^7 \text{ m}^{-1}$
Acceleration due to gravity,	$g$	$9.81 \text{ m/s}^2$
Atomic mass unit (1u)	$u$	$1.66 \times 10^{-27} \text{ kg}$
Avogadro's number	$N_A$	$6.023 \times 10^{23} \text{ mol}^{-1}$
Threshold of intensity of hearing	$I_0$	$1.0 \times 10^{-12} \text{ W/m}^2$
Coulomb constant	$k$	$8.988 \times 10^9 \text{ N.m}^2/\text{C}^2$
Permittivity of free space	$\epsilon_0/\kappa_0$	$8.85 \times 10^{-12} \text{ C}^2/\text{N.m}^2$
Permeability of free space	$\mu_0$	$4\pi \times 10^{-7} \text{ H/m}$

#### Energy equivalent of atomic mass unit:

One atomic mass unit (1.0 u) is equivalent to 931.5 MeV

Continued...

## APPENDIX II

### List of formulas

$$A_v = \frac{V_c}{V_b}$$

$$\alpha_{dc} = \frac{\beta_{dc}}{\beta_{dc} + 1}$$

$$\beta_{dc} = \frac{\alpha_{dc}}{1 - \alpha_{dc}}$$

$$B = \frac{\mu_0 I}{2\pi r}$$

$$B = \mu_0 n I$$

$$\xi = V + I r$$

$$\xi = b l v$$

$$\xi = -N \frac{\Delta \Phi}{\Delta t}$$

$$\xi = -L \frac{dI}{dt}$$

$$\xi = -M \frac{dI}{dt}$$

$$F = B I L \sin \theta$$

$$F = q v B \sin \theta$$

$$\frac{F}{\ell} = \frac{\mu_0 I_1 I_2}{2\pi d}$$

$$f_r = \frac{1}{2\pi \sqrt{LC}}$$

$$I_{tot} = \sqrt{I_R^2 + (I_L - I_C)^2}$$

$$I = n e A (v_n + v_p)$$

$$I = n e v_d A$$

$$I = I_{max} \sin \omega t$$

$$I_{rms} = \frac{I_{max}}{\sqrt{2}}$$

$$I_x = \left( \frac{R_T}{R_x} \right) I_T$$

$$L = \frac{N \Phi_B}{I}$$

$$L = \frac{\mu_0 N^2 A}{l}$$

$$M = \frac{N \Phi_B}{I}$$

$$M = \frac{\mu_0 N_1 N_2 A}{l}$$

$$P = IV = I^2 R = \frac{V^2}{R}$$

$$P_t = I_{rms} V_{rms} \cos \phi$$

$$P_r = V_{rms} I_{rms} \sin \phi$$

$$P_a = I_{rms}^2 Z$$

$$R = \frac{\rho L}{A}$$

$$R = R_0 [1 + \alpha (T - T_0)]$$

$$R_T = R_1 + R_2 + R_3 + \dots$$

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$

$$r = \frac{mv}{Bq}$$

$$\tau = N B I A \sin \theta$$

$$U = \frac{1}{2} L I^2$$

$$U = \frac{1}{2} B^2 A \frac{l}{\mu_0}$$

$$V_H = B v d$$

$$V = V_{max} \sin \omega t$$

$$V_{rms} = \frac{V_{max}}{\sqrt{2}}$$

$$V_x = \left( \frac{R_x}{R_T} \right) V_s$$

$$X_C = \frac{1}{2\pi f C}$$

$$X_L = 2\pi f L$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$\oint B \cdot dl = \mu_0 I$$

$$d\mathbf{B} = \frac{\mu_0 I}{4\pi} \frac{d\ell \times \hat{r}}{r^2}$$

$$\Phi_B = B A \cos \theta$$

$$\cos \phi = \frac{R}{Z}$$

$$\tan \phi = \frac{X_L - X_C}{R}$$

End of Page